
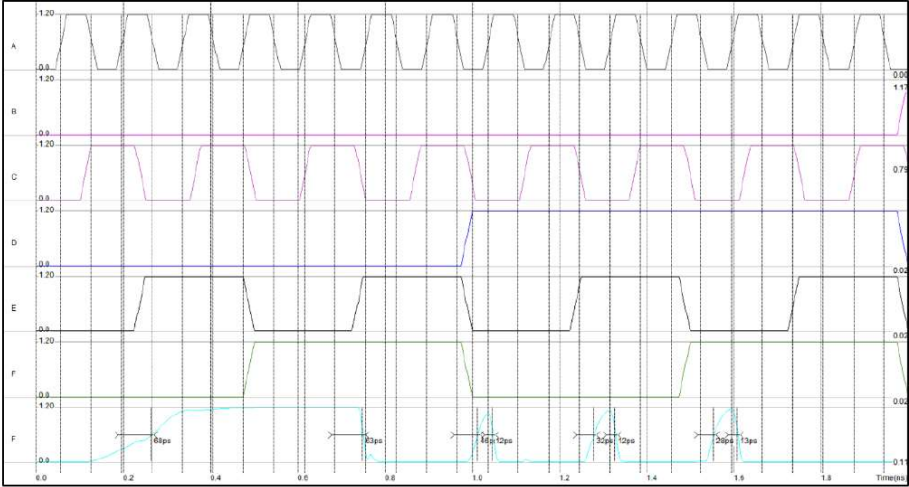


FUNCTION $F = \{(A + C) (B + D) + EF\}'$

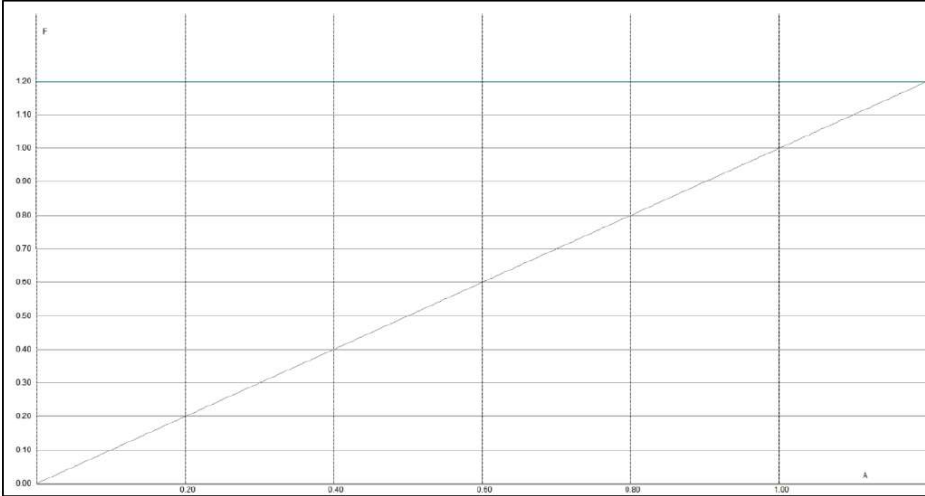

VOLTAGE VS TIME



VOLTAGE VS VOLTAGE